

Exercise 2: SystemC and Virtual Prototyping

SystemC Modules

Éder Zulian, Matthias Jung

WS 2017/2018


The source code to start this exercise is available here:

<https://github.com/TUK-SCVP/SCVP.Exercise2>

 Task 1

NAND Gate

In this task you will write your first SystemC module. The module should have the name `nand` and should implement the functionality of a NAND gate, shown below.




As input and output signals `sc_in` and `sc_out` should be used with the template type `bool`. The input and output signals should be initialized with a proper name in the `SC_CTOR`. The module should have one `SC_METHOD` called `do_nand()` which is sensitive to the input signals `A` and `B`. The module should be implemented in the file `nand.h`.

Task 2

SystemC Module Hierarchy – XOR

In this task you will write a SystemC module, which is composed out of other SystemC modules. The module should have the name `exor` and should implement the functionality of an XOR using only NAND gates, as shown below.

 In order to connect the `nand` modules, you need additional helping signals which you will implement by using the `sc_signal<bool>` datatype. The signals should have



the names h1,h2 and h3. All input, output and helping signals and the nand modules should be initialized properly with a name from the SC_CTOR(exor).

If you are done with the implementation, have a look at the SC_MODULEs stim and mon and the sc_main() function and try to understand what these components are doing.

Why is the stim class using an SC_THREAD for its process and not a SC_METHOD?

Now lets compile and run your program. If you did everything correctly, you should see the following output:

time	A	B	F
0 s	0	0	1
0 s	0	0	0
10 ns	0	1	0
10 ns	0	1	1
25 ns	1	0	1
35 ns	1	1	1
35 ns	1	1	0
45 ns	0	0	0

Why are you seeing several outputs for each time, sometimes even with wrong results?


Task 3

Debugging Tracing

Additionally to the mon component, use the waveform feature of SystemC in the sc_main method before sc_start. Then use the tool GTKWave in order to have a look on the waveform.

Information on this feature can be found here: <https://www.doulos.com/knowhow/systemc/tutorial/debugging/>

In GTKWave you have to drop the signals to the waveform and you have to zoom out a little in order to see the final result:

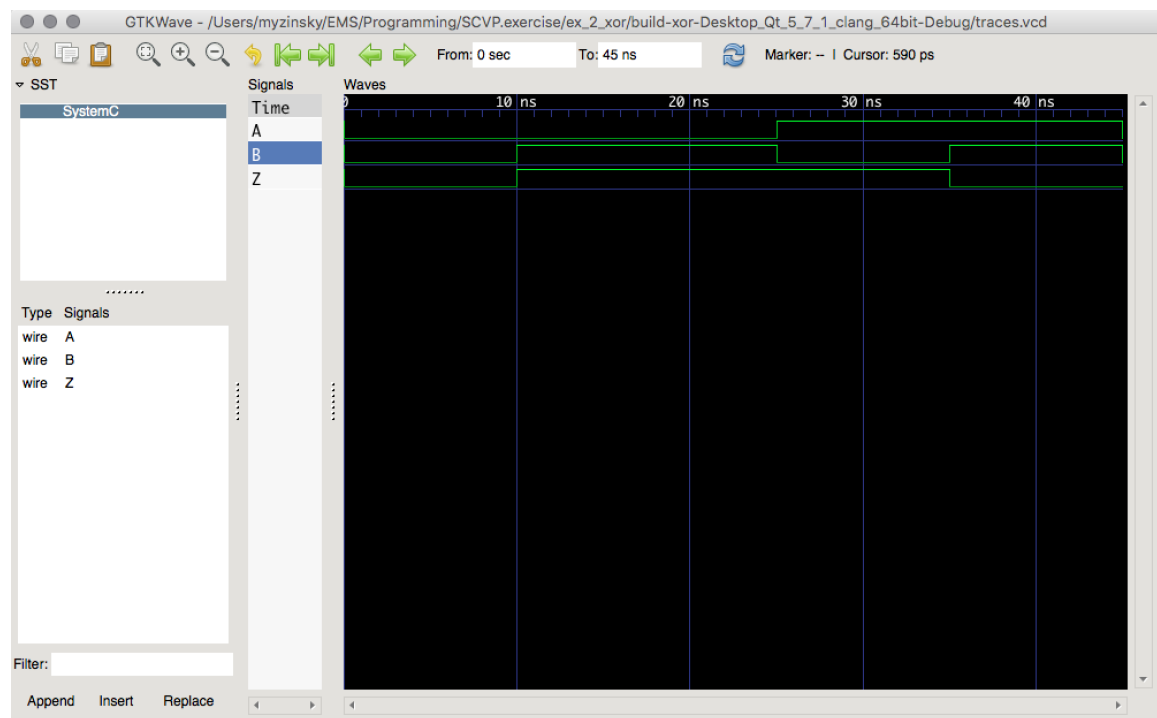

Task 4

Clocked Processes

Add a `sc_clock` to the `sc_main` function. Remove the `wait(XX, SC_NS)` statements in the `stim` module and replace them by normal `wait()` statements. Add to the `stim` and the `mon` components an `sc_in<bool> Clk` and make both processes of the modules only sensitive to the positive edge of the clock. Then connect the `sc_clock` in the `sc_main` to the modules. What you will observe at the terminal output?